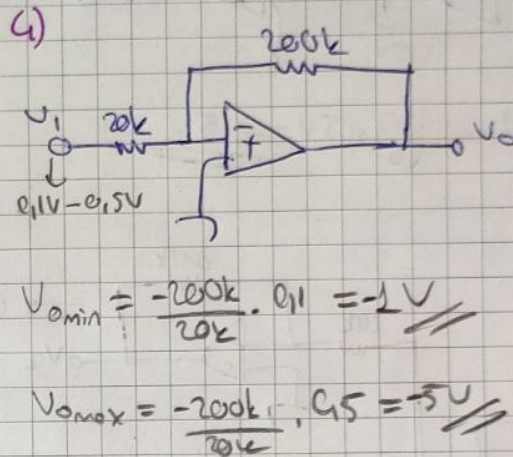
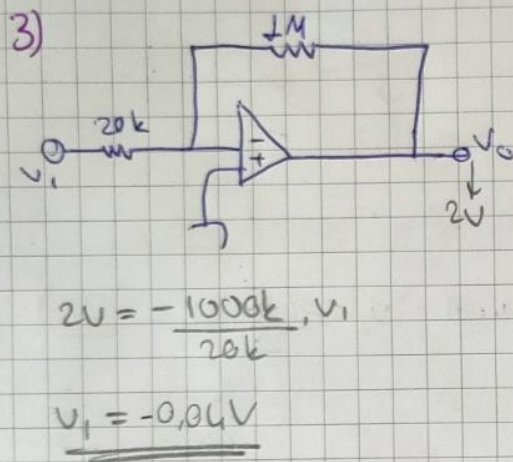
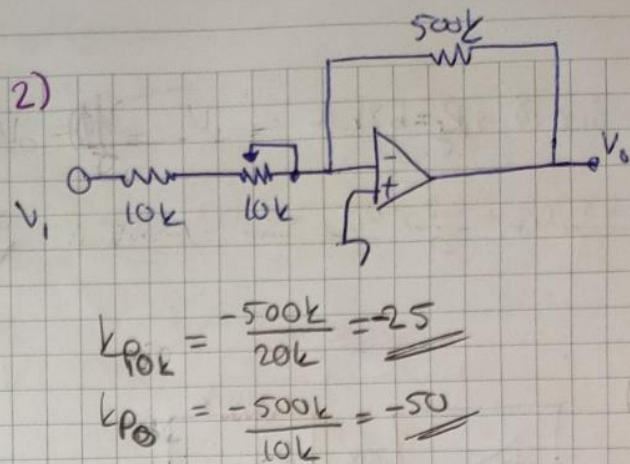
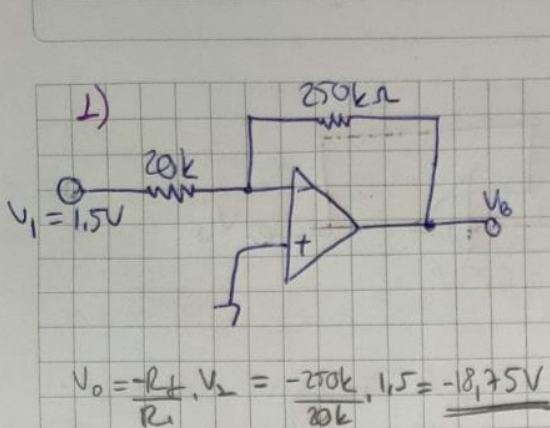


6)

$$V_o = 2.4 \Rightarrow$$


$$2.4 = \left(1 + \frac{360}{12}\right) \cdot V_1$$

$$V_1 = 0.077V$$

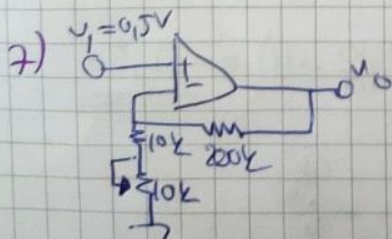7)


$$V_1 = -3V \Rightarrow \left(1 + \frac{R_f}{R_i}\right) \cdot V_1 = V_o$$

$$V_o = \left(1 + \frac{360}{12}\right) \cdot V_1 = -9.3V$$



$$V_{o0} = \left(\frac{200}{10} + 1\right) \cdot 0.5 = 10.5V$$

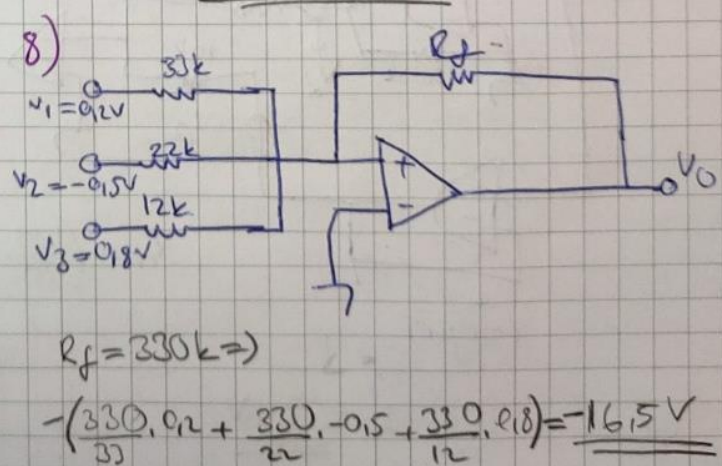
$$V_{o_{10k}} = \left(\frac{200}{20} + 1\right) \cdot 0.5 = 5.5V$$



9) $\text{örn: } 8 \rightarrow R_f = 68k\Omega$


$$-\left(\frac{68}{33} \cdot 0,2 + \frac{68}{22} \cdot 0,5 + \frac{68}{12} \cdot 0,8\right) = \underline{\underline{-3,4V}}$$

10)

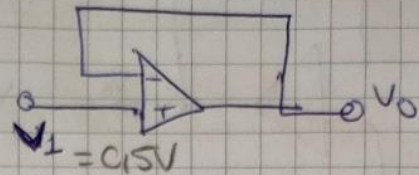


$V_0 = 0,5V$ izleyici devresi

12)

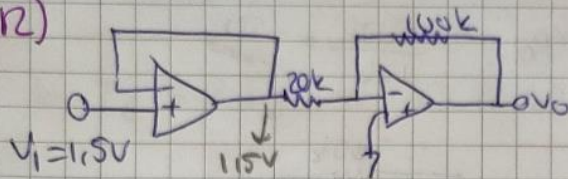

$$V_0 = -\frac{100}{20} \cdot 1,5V = \underline{\underline{-7,5V}}$$


13)

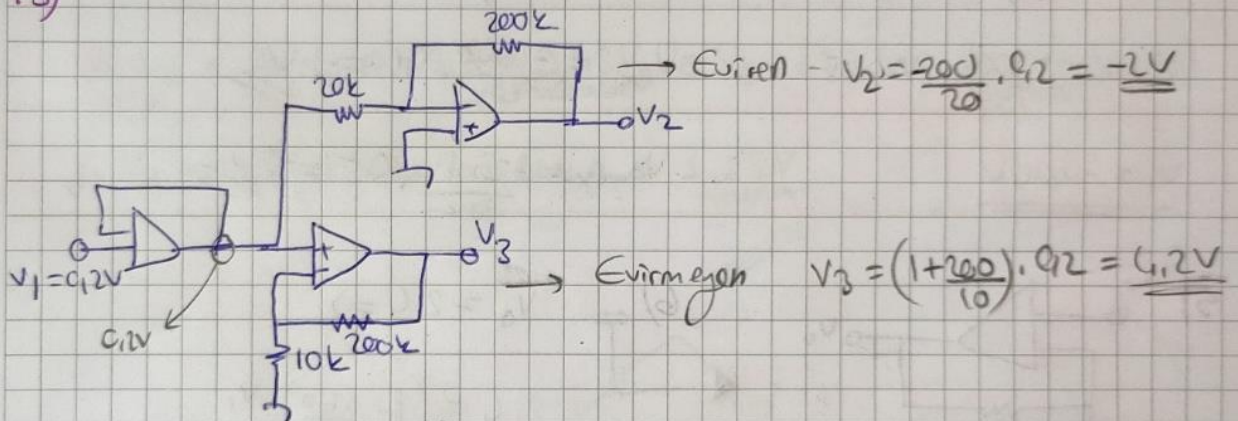

Eğerden $V_2 = \frac{200}{20} \cdot 0,2 = \underline{\underline{-2V}}$

Eğerden $V_3 = \left(1 + \frac{200}{10}\right) \cdot 0,2 = \underline{\underline{4,2V}}$


14) $V_1 = 0,1V$

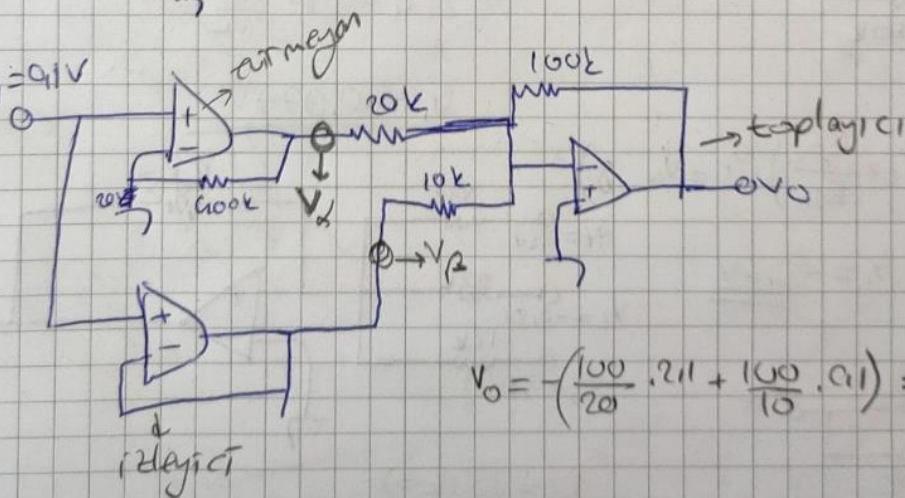

$$V_0 = -\left(\frac{100}{20} \cdot 2,1 + \frac{100}{10} \cdot 0,1\right) = \underline{\underline{-11,5V}}$$

$$V_1 = \left(1 + \frac{400}{20}\right) \cdot 0,1 = \underline{\underline{2,1V}}$$

$$V_2 = \underline{\underline{0,1V}}$$

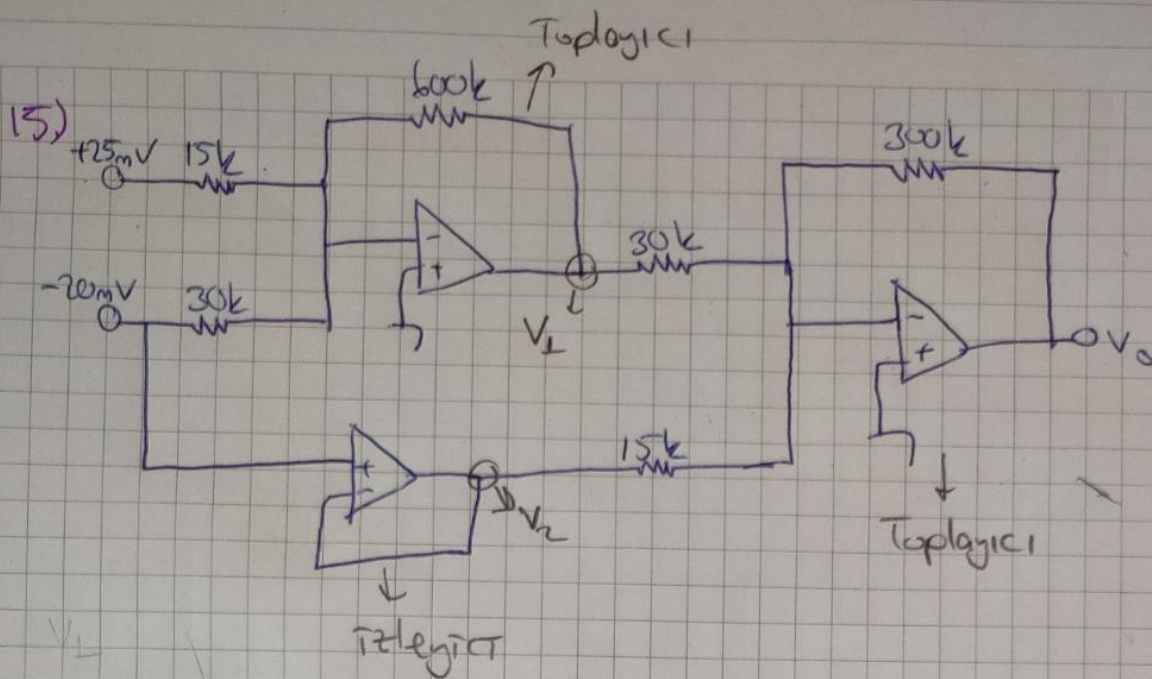

$$V_1 = -\left(\frac{600}{15} \cdot 0,025 + \frac{600}{30} \cdot -0,02\right) = \underline{\underline{-0,6V}} \quad V_2 = \underline{\underline{-0,02V}}$$

$$V_0 = -\left(\frac{300}{30} \cdot -0,6 + \frac{300}{15} \cdot -0,02\right) = \underline{\underline{6,4V}}$$