

$$a) I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{16 - 0.7}{510k} = \underline{30 \mu A} \quad (2)$$


$$b) I_{CQ} = 170 \cdot 30 \mu A = \underline{3.6 mA} \quad (2)$$

$$c) V_{CEQ} = V_{CC} - I_C \cdot R_C = 16 - 3.6 mA \cdot 1.7k = \underline{9.52V}$$

$$d) V_C = \underline{9.52V}$$

$$e) V_B = \underline{0.7V}$$

$$f) V_E = \underline{0V}$$

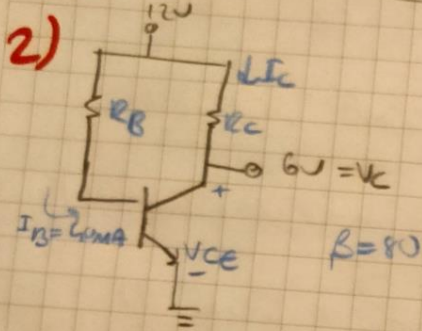


$$a) I_C = I_B \cdot \beta \Rightarrow 80 \cdot 40 \mu A = \underline{3.2 mA}$$

$$b) R_C = \frac{V_{CC} - V_C}{I_C} = \frac{12 - 6}{3.2 mA} = \underline{1.875 k\Omega}$$

$$c) R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{12 - 0.7}{40 \mu A} = \underline{282.5 k\Omega} \quad (2)$$

$$d) V_{CE} = \underline{6V}$$

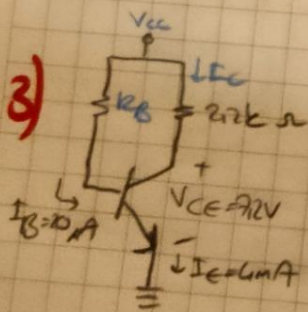

$$a) I_C = I_E - I_B \Rightarrow 4 \mu A - 20 \mu A = \underline{3.98 mA}$$

$$b) V_{CC} = I_C \cdot R_C + V_{CE} = 3.98 mA \cdot 2.2k + 7.2 = \underline{15.956V}$$

$$c) \beta = \frac{I_C}{I_B} = \frac{3.98 mA}{20 \mu A} = \underline{199} \quad (2)$$


$$d) R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{15.956 - 0.7}{20 \mu A} = \underline{762.8 k\Omega}$$

4) sorul'daki $\rightarrow I_{C_{sat}} = \frac{V_{CC}}{R_C} \quad \frac{I_C}{118k} = \underline{\underline{8,88mA}}$ (1)

5) a) $I_C = \frac{V_{CC}}{R_C} = \frac{21}{3k} = \underline{\underline{7mA}}$ b) $R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{21 - 0,7}{25\mu A} = \underline{\underline{812k\Omega}}$

c) $I_{CQ} = \underline{\underline{3,5mA}} \quad V_{CEQ} = \underline{\underline{10,5V}}$ d) $\beta = \frac{I_C}{I_B} = \frac{3,5mA}{25\mu A} = \underline{\underline{140}}$

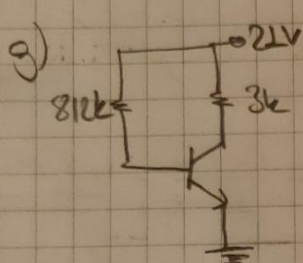e) $\alpha = \frac{\beta}{\beta + 1} = \frac{140}{141} = \underline{\underline{0,983}}$ f) $I_C = \frac{V_{CC}}{R_C} = \frac{21}{3k} = \underline{\underline{7mA}}$ (5)



h) $P_D = V_{CE} \cdot I_C = 10,5 \cdot 3,5mA = \underline{\underline{36,75mW}}$


i) $P_S = V_{CC} \cdot (I_B + I_C) = 21 \cdot (25\mu A + 3,5mA) = \underline{\underline{74mW}}$

j) $P_D - P_S = 74 - 36,75 = \underline{\underline{37,25mW}}$

6) a) $V_{CE} = V_{CC} - I_C \cdot R_C \Rightarrow I_C = \underline{\underline{8,88mA}}$
 $0 = 16V - I_C \cdot 118k$


b) $= f\left(\frac{V_{CE}}{2}, \frac{I_C}{2}\right) = \underline{\underline{Q(8V, 4,45)}}$ (8)

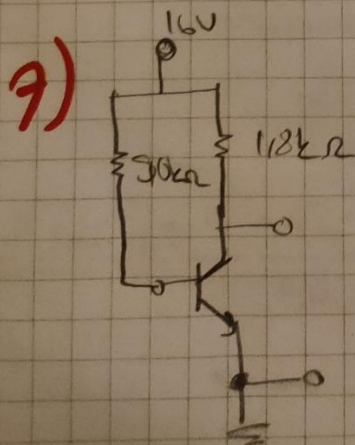c) $\beta = \frac{I_C}{I_B} \quad \beta = \frac{4,45}{30\mu A} = \underline{\underline{148}}$



$I_C = \beta \cdot I_B = 148 \cdot 14,06\mu A = \underline{\underline{2,102mA}}$

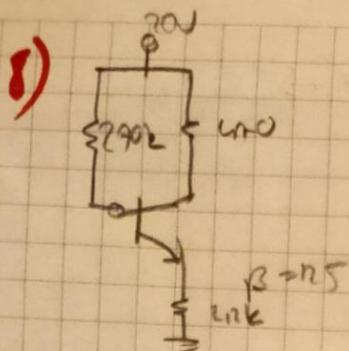$V_{CE} = 16 - 2,102 \cdot 118 = \underline{\underline{12,36V}}$



a) $I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} = \frac{20 - 0.7}{2k + 126 \cdot 1k} = \underline{\underline{35 \mu A}}$

b) $I_C = \beta I_B = 125 \cdot 35 \mu A = \underline{\underline{4.375 mA}}$

c) $V_{CE} = V_{CC} - I_C (R_C + R_E) = 20 - 4.375 (2k + 1k) = \underline{\underline{8.132 V}}$


d) $V_C = V_{CC} - I_C R_C = 20 - 4.375 \cdot 2k = \underline{\underline{11.84 V}}$

e) $V_E = I_E R_E = 4.375 \cdot 1k = \underline{\underline{4.375 V}}$

f) $V_B = \frac{V_{CC} R_E}{R_B + R_E} = \frac{20 \cdot 1k}{2k + 1k} = \underline{\underline{6.67 V}}$

2) a) $I_C = \beta I_B = 125 \cdot 28 \mu A = \underline{\underline{3.5 mA}}$ b) $Q(10V, 3.5 mA)$

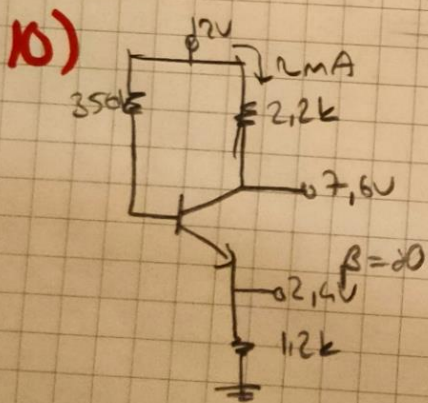c) $\beta = \frac{I_C}{I_B} = \frac{3.5 mA}{28 \mu A} = \underline{\underline{125}}$ d) $\beta = 125$



a) $R_C = \frac{V_{CC} - V_C}{I_C} = \frac{12 - 7.6}{2mA} = \underline{\underline{2.2 k\Omega}}$

b) $R_E = \frac{V_E}{I_E} = \frac{2.4}{2mA} = \underline{\underline{1.2 k\Omega}}$

c) $I_C = \beta I_B \Rightarrow 2.80 \cdot I_B \Rightarrow I_B = \underline{\underline{25 \mu A}}$

d) $V_{CE} = 5.2 V$

e) $V_B = 3.1 V$

11) a) $\beta = \frac{3100}{20 \mu A} = \underline{155}$ b) $V_{CE} = V_C + I_C R_C = \underline{17.75 \text{ V}}$

c) $R_B = \frac{17.75 - 2.0}{20 \mu A} = \underline{747.5 \text{ k}\Omega}$

12) $I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E} = \frac{20 - 0}{9.4 \text{ k}\Omega} = \underline{2.13 \text{ mA}}$

13) a) $I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E} = \frac{4 = 24 - 10}{12 \text{ k}\Omega + 12 \text{ k}\Omega} = \underline{R_C = 2.3 \text{ k}\Omega}$

b) $\beta = \frac{4 \text{ mA}}{30 \mu A} = \underline{133}$

c) $I_B = \frac{V_{CC} - V_{BE}}{R_B + R_{E,B}} \Rightarrow 30 \mu A = \frac{24 - 0.7}{R_B + 12 \text{ k}\Omega}$

$\underline{R_B = 617 \text{ k}\Omega}$

(OK)